

[illegible]

NEWS OF AMATEUR RTTY

RTTY



This page of the Bulletin is for use of amateurs who have RTTY EQUIPMENT FOR SALE OR TRADE and those looking for equipment to buy or trade. It is a free service and may be the means of getting someone on the air.

WANTED: Model 14 TD.....W6PCF
WANTED: Aug. '55, Jan., Apr., Aug '56, RTTY.....K4KKZ
WANTED: Information on FC#CI-ZA/CAN 9367 FEF.....K4KKZ
FOR SALE: Model 12, trade on Tape gear.....W9HKA
FOR SALE: Model 15 complete with table.....Robert C. Clark,
Box 1244, 5050 Comm Maint Sq. APO 942 Seattle.
WANTED: August 1953 and October 1954 RTTY.....W8LEX
FOR SALE: 26 type pallett conversion kits (\$8.00).....W9GRW
FOR SALE: ARC-4 Two meter with rack and
dynamotor, very clean.....K6GJM

FOR SALE: Complete Station, 522 trans. & Rec., T. U. with 7" scope mounted in Bud relay rack cabinet. W6CMQ

RTTY, Inc.
372 WEST WARREN WAY
Arcadia, California 91759
Return Postage Guaranteed

Modification of Collins KWS-1 for Frequency Shift Keying

BY FRANK C. WHITE, W3PYW

The Collins people tell you you can get frequency shift keying out of the KWS-1 by putting in two-tone audio, and they are right. I tried it about a year and a half ago and was fairly well pleased with the results. Only trouble is, you gotta be careful about what you are doing if you do not want a billet doux from the Fox Charlie Charlie.

Some folks call me ingenious, my wife says I am lazy. I think she is right, cause I am always looking for an easier (often better) way of doing things. You would not think there would be an easier way of creating fsk with a KWS-1 than just putting in the two-tone audio, but let me assure you there is (almost that is).

Most of the fellows have the 2125 cps and 2975 cps audio tones to use for creating the fsk with the KWS-1. The audio of the KWS-1 is made so it passes 3000 cps and droops real fast thereafter. Some KWS-1 units droop before the 3000 cps is reached — and 2975 is near 3000 cps. Here is the way you find out if yours does. Put the 2125 tone into the KWS-1 and observe the final amplifier plate current. Then shift the audio to 2975 and observe the plate current. If the plate current drops off, you have "droop trouble." Two KWS-1 of three, (that I have observed in this manner) had less output at 2975 than at 2125; this puts "bias" in your teletype signal, and you are started for trouble.

What if the two-tone audio you put in does not have the same amplitude on mark as it does on space — more bias

What if the audio is not pure sine wave? More trouble. You have spurious signals, and the FCC writes you a QSL card.

Not for any friend that asks me for advice, shifting the oscillator is the "easy" way. Let us see how to go about doing it.

If you have a 26, or 15, or other type of single magnet printer, put a polar relay in series with the printer magnet. The polar relay will then be available to key a stabilized DC source to use for creating FSK. When I said stabilized, I meant stabilized. Use a VR tube and stabilize to 150 volts DC. The frequency shifter is a 6AL5. Yes, I said 6AL5. Do not use a 1N34 germanium unless you want more trouble. Build up the diode shifter in a small metal box, Mini Box has a "standard" item that fits o.k. Put the potentiometer on the box in such a way it is accessible when the box is bolted in place in the KWS-1. The metal box is bolted against the side of the RF shield cover of the KWS-1 by loosening one of the existing screws and slipping the lip of the box under it (see drawing). Obtain the filament voltage from the dial light circuit (two 6" leads).

The output of the diode shifter is a 20mmf mica condenser. Tie a small wire to this and run it over to the grid pin of the oscillator (V001). Pull the oscillator tubes, wrap the small wire around the grid pin (No. 1), and plug it back in the socket.


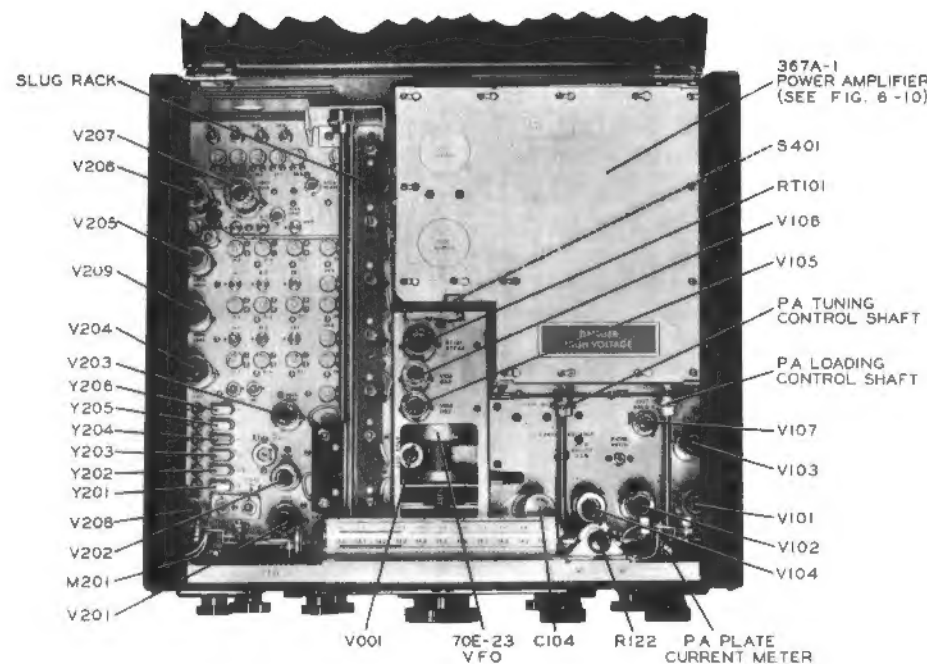


Figure 6-2. Exciter/Power Amplifier, Top View, Top Cover Open

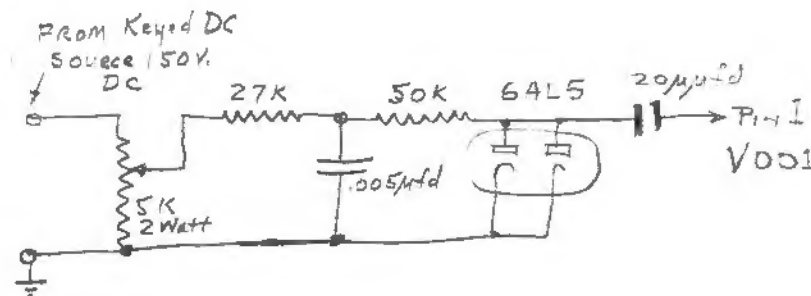


You will find that stray capacity (added in this way) moves the oscillator frequency about 15kc. This error cannot be corrected by using the rotatable index. Loosen the allen screws on the shaft of the VFO (where it connects to the dial drive) and correct for this change, so that the movable index is at the middle of the window. If the entire modification takes you more than half an hour, you are a slow poke.

Setting the shift is a breeze. Just adjust the potentiometer with a space sig-

nal in your converter (voltage on the potentiometer). The adjustment is smooth as silk and can be set to anything from zero to about 900 cps. Another feature of accomplishing the PSK in this manner is that the shift is correct for 40-20 or 80 meters once it is set for one band.

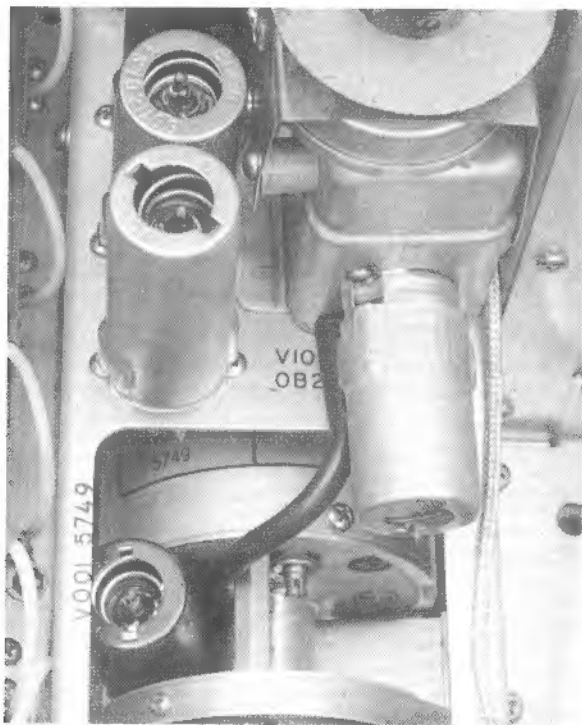You will note that the entire modification is one that can be removed easily if (and when) you decide to peddle your KWS-1 — but who is selling them? Wish I had one too.



The 6AL5 is mounted on the side of a 1 1/4" x 1 1/4" shield can. The potentiometer (and dial) are mounted atop the can. The capacity, coupling the 6AL5 diodes to the VFO (V001) grid is formed by the RG58U or RG59U coax, which may be seen running out of the bottom of the can to the VFO grid.

DESCRIPTION FSK OSCILLATOR, Courtesy VK-3-KF

BY FORREST CASTLE, (KR6AK) OKINAWA

The 12AU7 tube circuit is somewhat similar to a locked multi-vibrator. The feedback being adjusted by the coupling C and anode loads around the tube to the point where the crystal takes charge. The values shown are suitable for crystals between 2 and 4 Mes.

In series with the crystal is an LC network, which for the purpose of operation with our form of FS is essentially inductive in character if the point "X" in circuit diagram is shorted to ground the crystal oscillates at its natural freq. and when the short is removed the crystal oscillates either higher or lower in frequency depending on the character of the series reactance. We use essentially XL cut.

The variable capacitor shunted across L is used to adjust the amount of frequency shift to the desired value, depending on the number of frequency multiplier stages following the oscillator. With a crystal having good activity, a shift at the fundamental frequency of well over 1 KC can be achieved.

The .02 mfd mica condenser between the crystal and the LC network should be of good quality in the interest of stability and of low reactance at the operating frequency.

The crystal diode and 6J6 tube shunted across the LC network provide the Mark and Space keying facilities in practice, negative bias is applied to the grid of the tube through RA of sufficient amplitude to bias the tube to cut off when the keying line is open. With the tube at cut off, the crystal diode is not conducting and the shunting effect across the LE network is at a mini-

mum. This allows the reactance of the network to be effectively in series with the crystal, so shifting its frequency from its normal oscillating frequency to one determined by the effective reactance of the network. Now, application of a positive voltage to the grid of the 6J6 tube bucks the standing negative voltage and causes the tube and consequently the diode to conduct, so placing a partial short circuit across the LC network provided by the .001 capacitor in parallel with the 6J6 tube. This in effect brings the bottom of the crystal almost to ground potential and consequently it oscillates at almost the same frequency as it would when point "X" is metallically brought to ground. The difference in frequency between metallic and electronic ground varies with crystals but it has been found that it is about 100 CPS at about 3.5 Mes.

The positive voltage applied by keying should be of such magnitude as to cause the 6J6 to draw not less than 4MA and 5MA is quite effective. The value of the capacitor between the grid of the 6J6 and ground should be as small as possible consistent with the reduction of key thumps in adjacent channels. The clicks can be bad with crystals having marginal activity. Without any C the keyed waveform is as follows: No. 1 without C, No. 2 with C added.



Midwest Amateur Radio

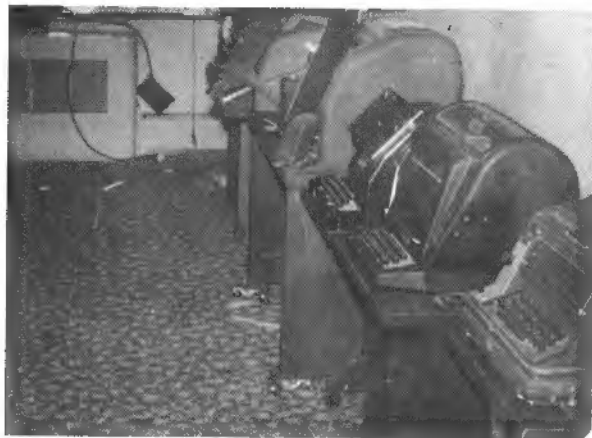


Fig. 1



Fig. 2



Fig. 3

Teletypers Society, Inc.

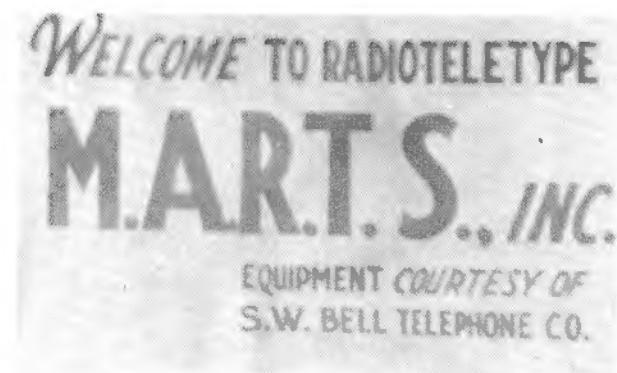


Fig. 4



Fig. 5



Fig. 6

Rare Rtty Stations



W7YZQ/7 at Idaho Convention



W7PSO at Casper Wyo.



W1PIL at Worchester, Mass.



W2VLL at Keyboard